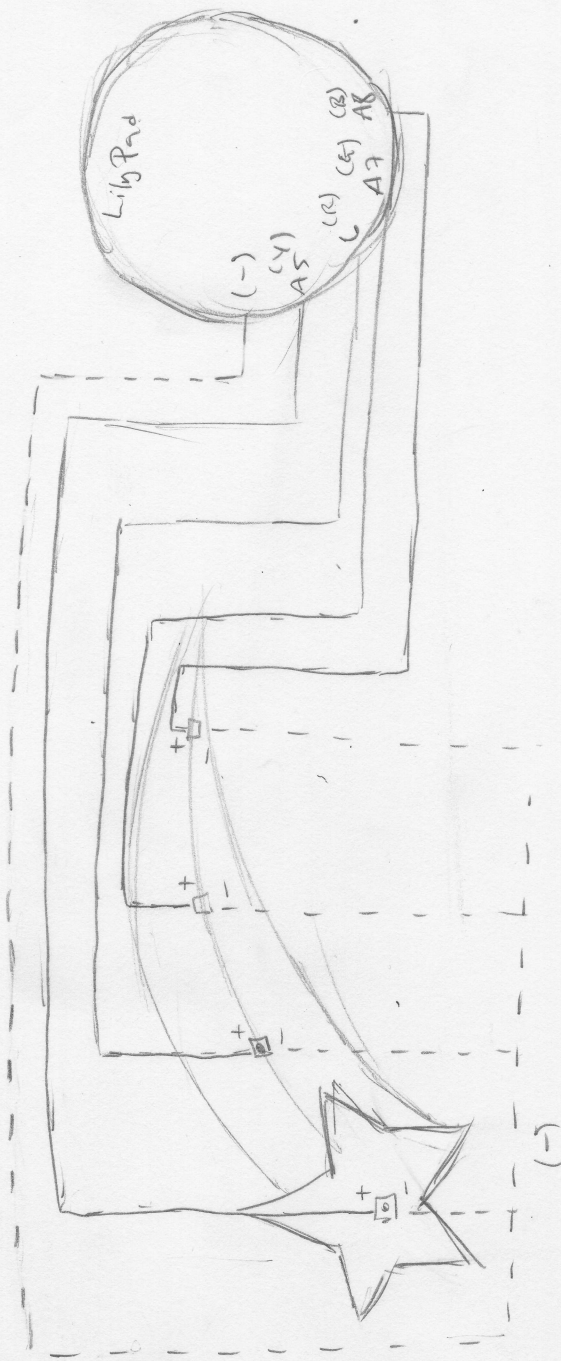


LilyPad Shooting Star Circuit




note: kids can customize color scheme

work w/ code to structure w/ if-else statements

Heart Shape Circuit

note: use 8 LEDs for simplicity.

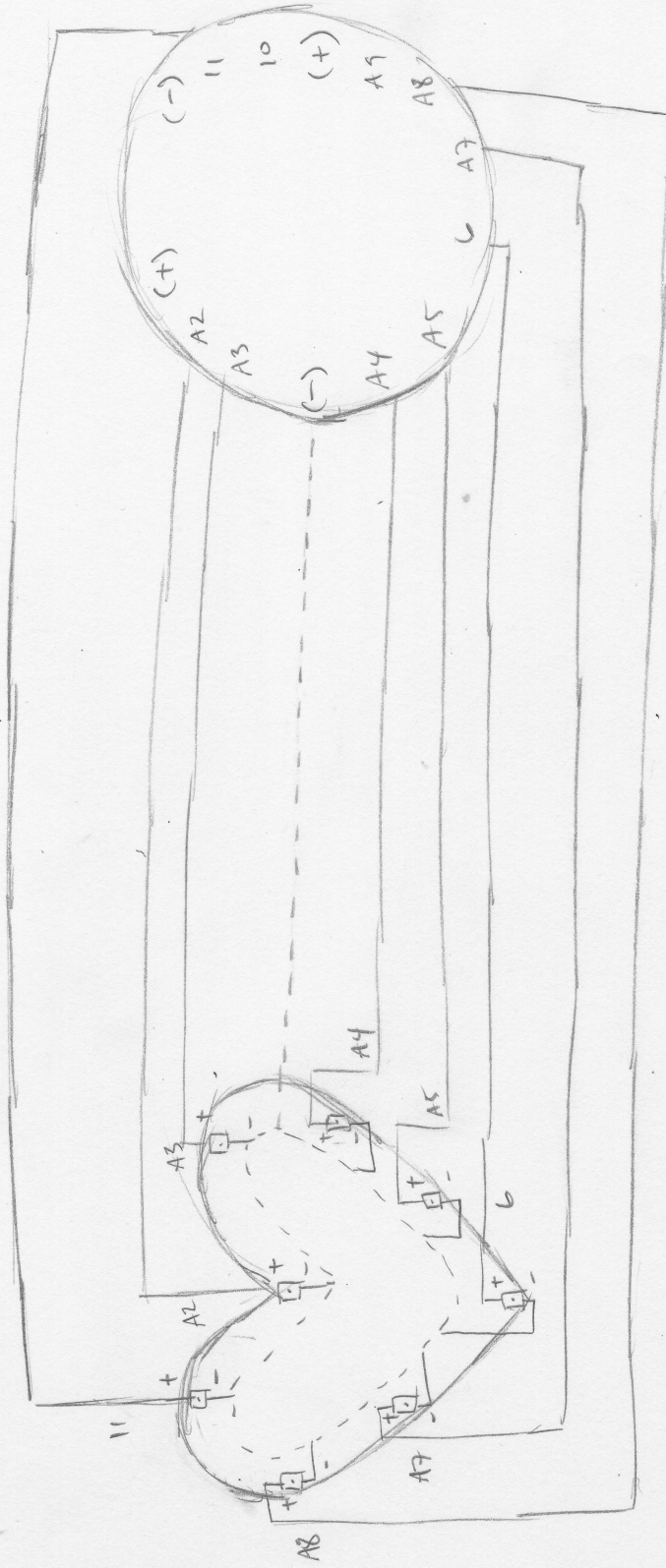

note: kids can choose sequential flashing or simultaneous structure code for Alternate flashing, different delays?